



Design Log – Electrical Circuits

Name: _____

Team: _____

Sketch the electrical circuit below.

Calculations

1) Does the electrical circuit work? If not, what one change (remember debugging a system requires one change at a time) do you plan to make first?

2) What problems were encountered and overcome by the team to achieve a successful circuit?